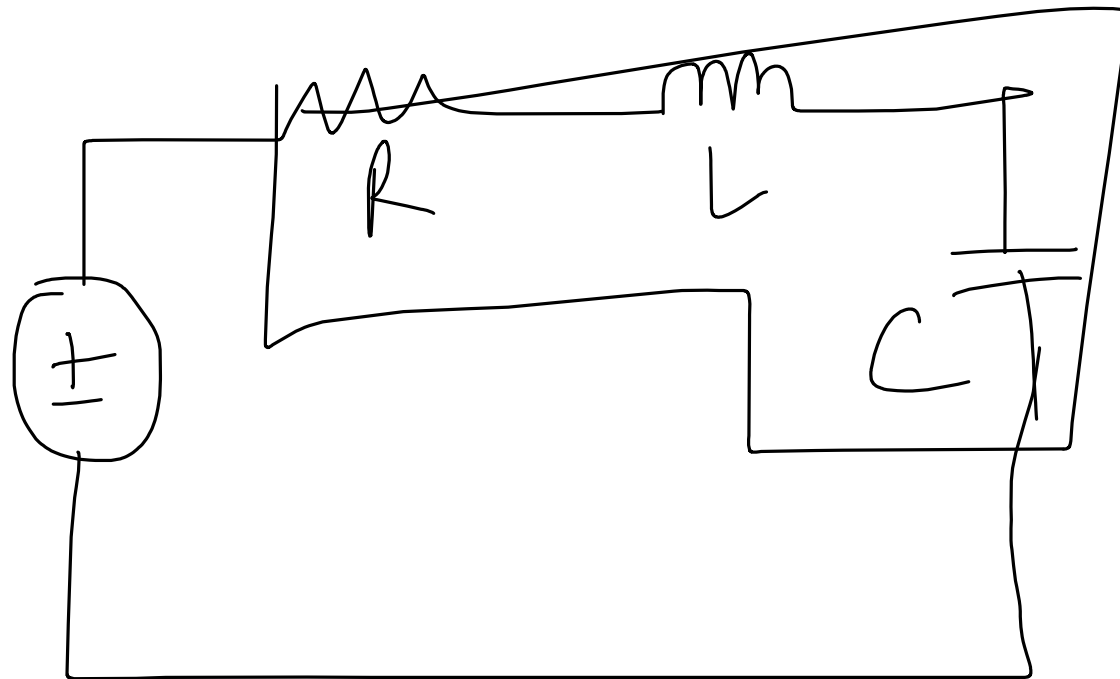


Series Resonance



Series
RLC circuit

$$L \rightarrow Z_L$$

$$C \rightarrow Z_C$$

$$Z = R + j \left(\omega L - \frac{1}{\omega C} \right)$$

Special Condition

resonance

$$\text{Im}(Z) = 0$$

$$\omega L - \frac{1}{\omega C} = 0$$

$$\Rightarrow \omega^2 = \frac{1}{LC}$$

$$\therefore \omega_0 = \frac{1}{\sqrt{LC}}$$

$$Z = R + j(\omega L - \frac{1}{\omega C})$$


$$Z = R$$



$$V = \frac{1}{R}$$

more energy
efficient

At resonance Condⁿ

$$\text{Im}[Z] = 0$$

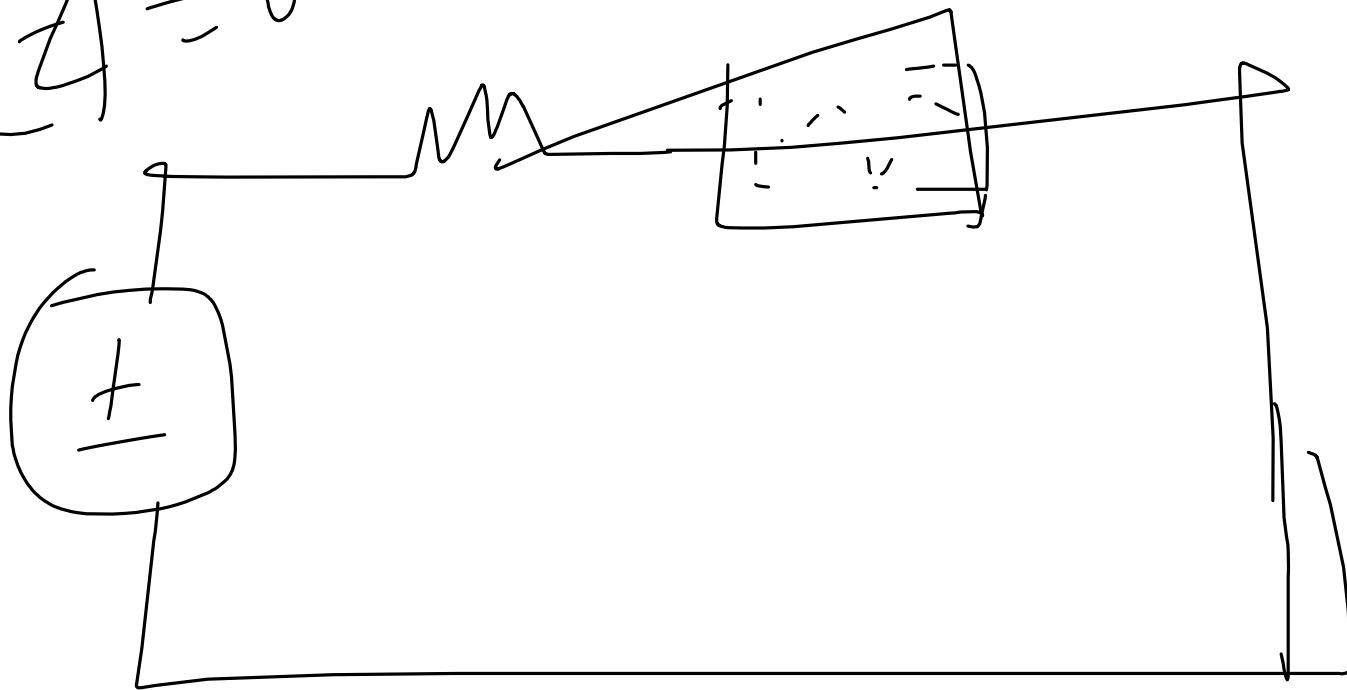

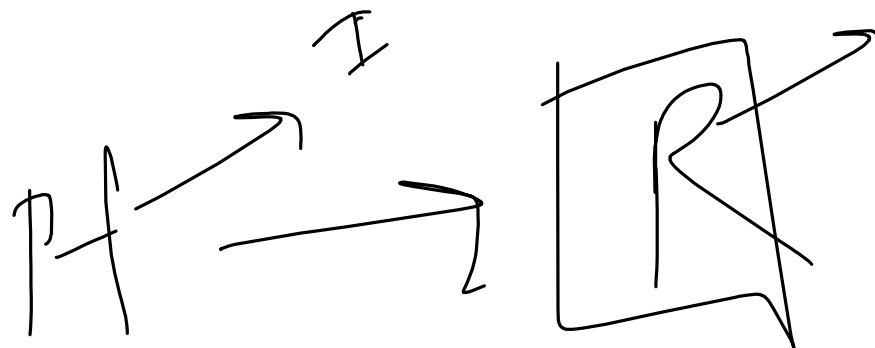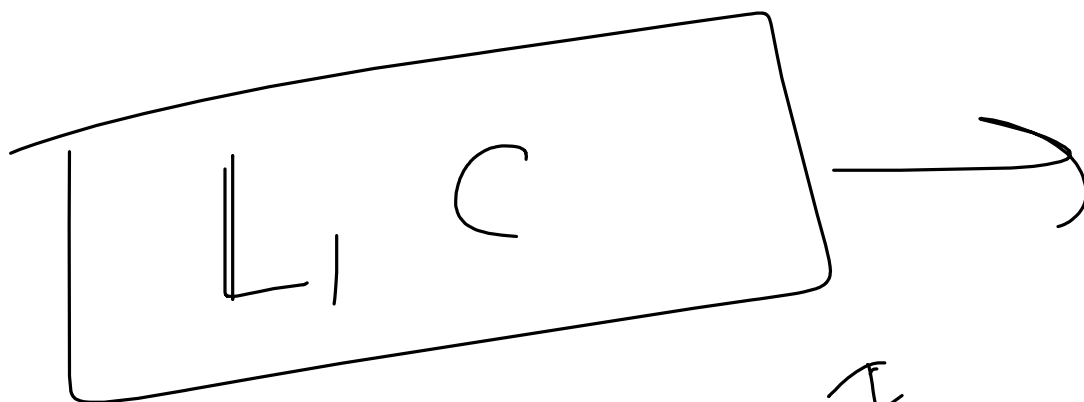


✓ ① Energy Efficiency

$$z = R$$

②

$$P f \rightarrow \frac{1}{P} \leq 1$$

$$Q = 0$$

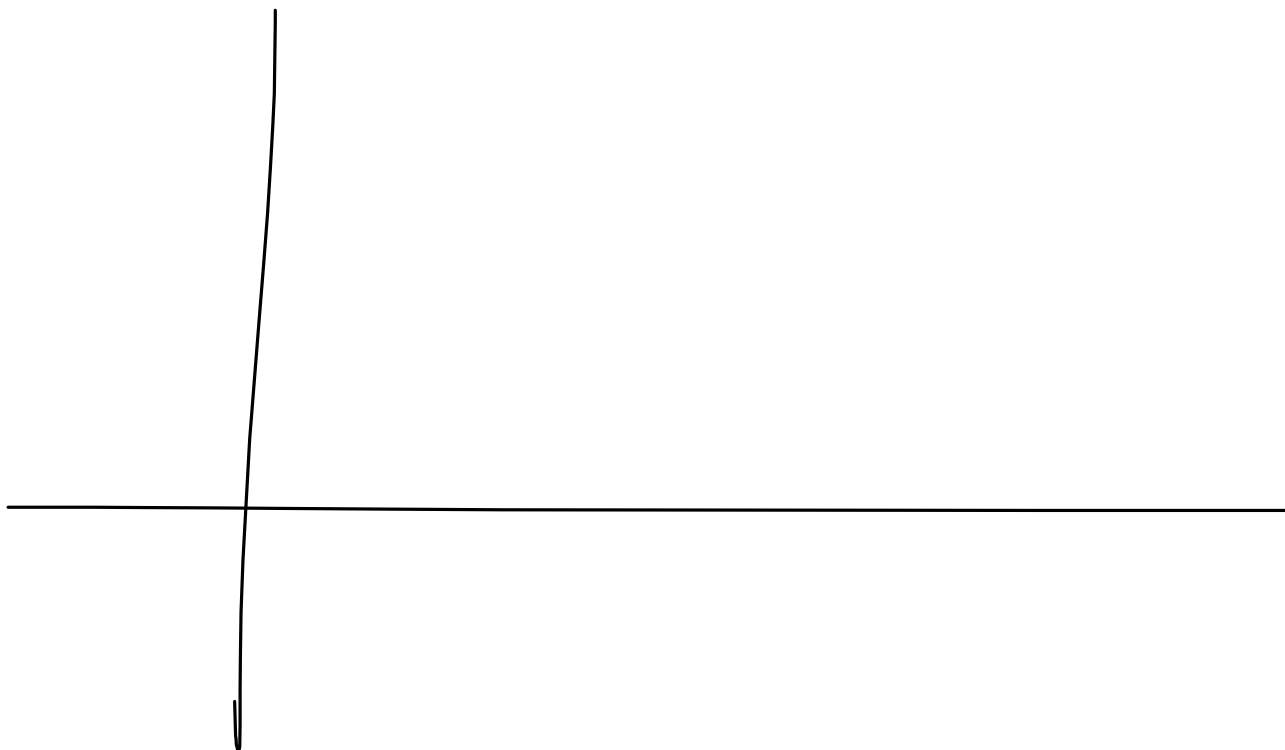


$$Z = R + j \left(\omega L - \frac{1}{\omega C} \right)$$

constant

$$V = I R$$

$$|I| =$$

$$|V| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}$$

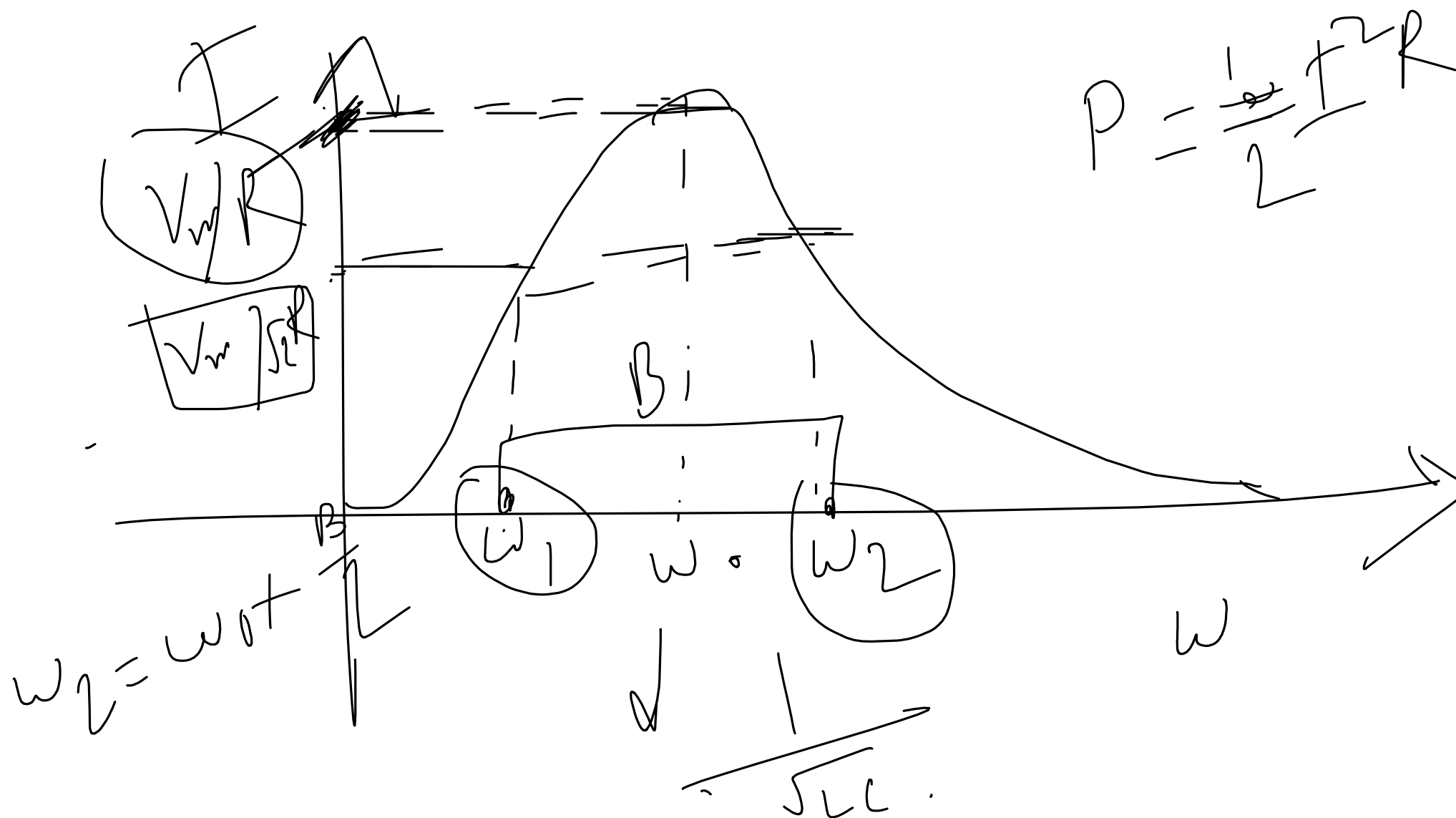

Solving for ω , we obtain

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$
$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$


(1)

half frequencies
 $\omega_0 \rightarrow$ central freq.
Resonant ω


$$\omega_0 = \sqrt{\omega_1 \omega_2}$$


$$\omega_2 - \omega_1 = \beta$$

Quality factor $\rightarrow Q$

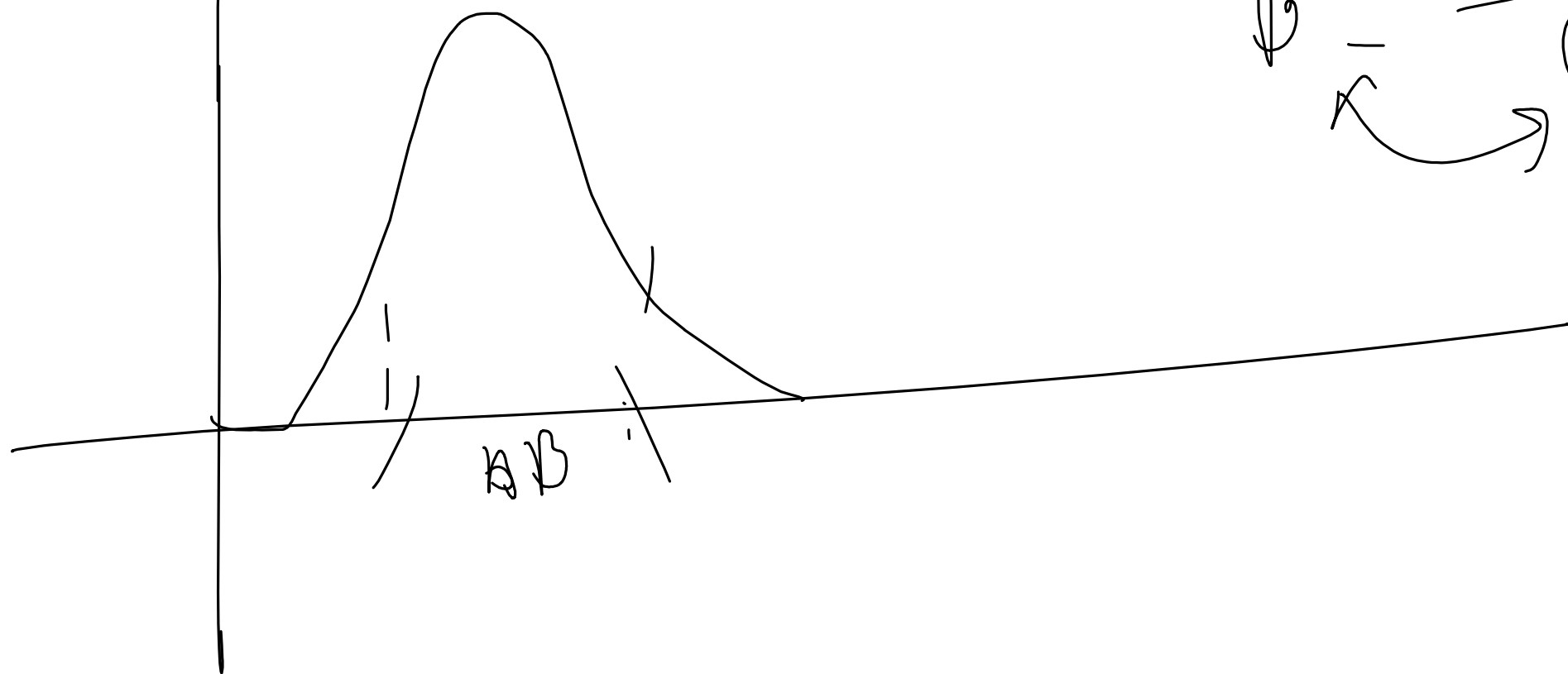

$$Q = \frac{\omega}{\Delta\omega}$$

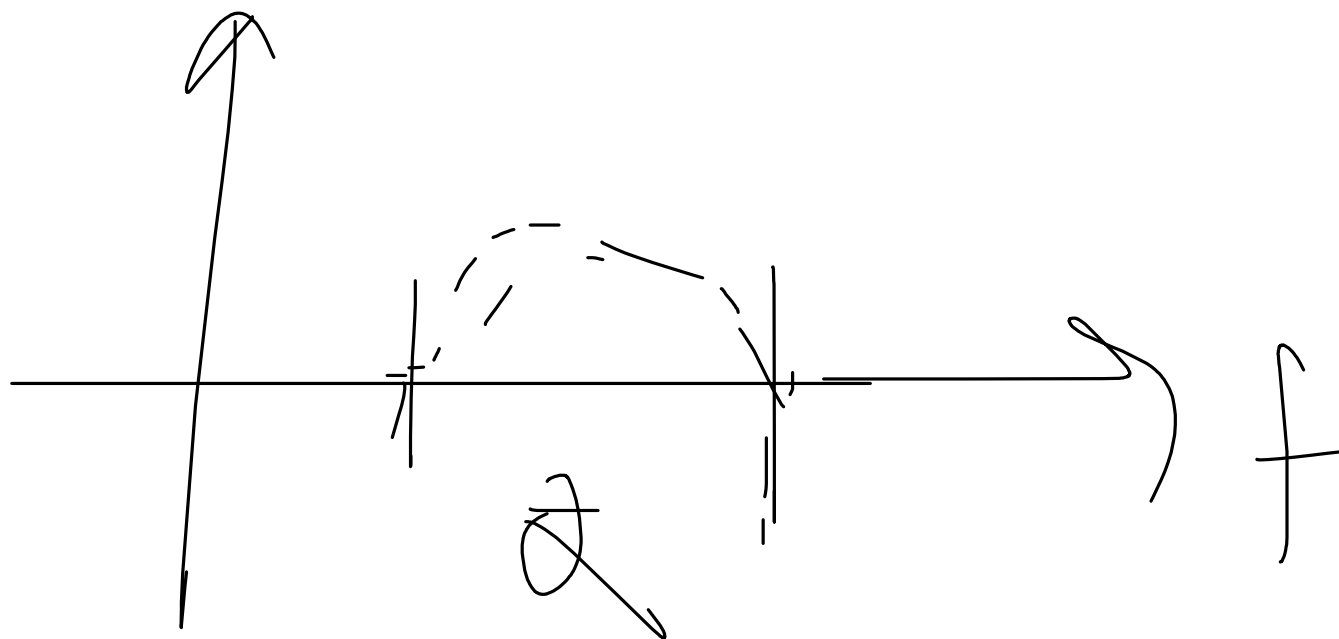

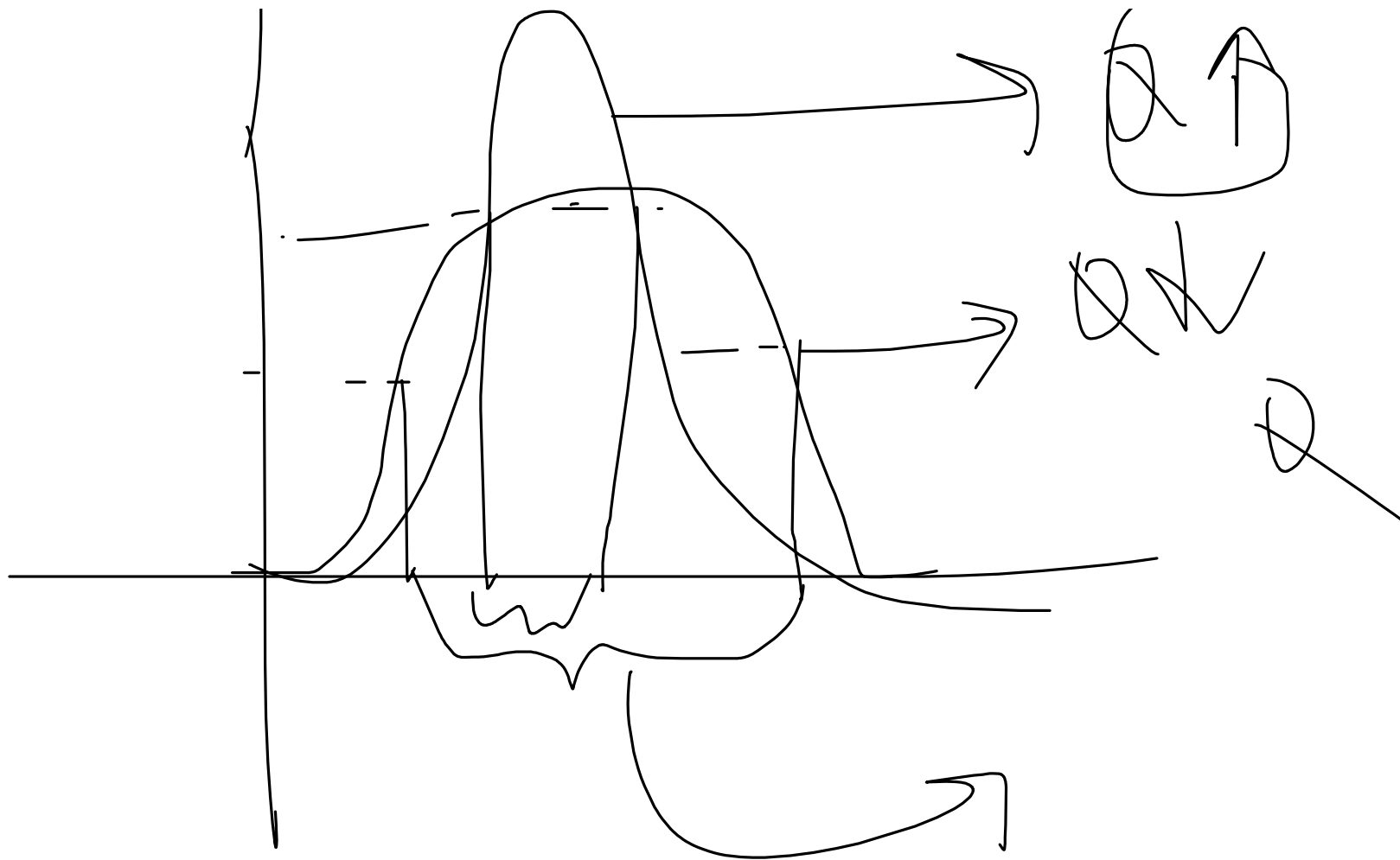

$$\textcircled{Q} = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R}$$

$$\rightarrow B = \frac{\omega_0}{Q}$$

Practice Problem 14.7

A series-connected circuit has $R = 4 \Omega$ and $L = 25 \text{ mH}$. (a) Calculate the value of C that will produce a quality factor of 50. (b) Find ω_1 , ω_2 , and B . (c) Determine the average power dissipated at $\omega = \omega_0$, ω_1 , ω_2 . Take $V_m = 100 \text{ V}$.

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Here,

$$Q = 50$$

$$Q = \frac{1}{\omega_0 CR}$$


$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 CR}$$

Since the quality factor is dimensionless. The relationship between the bandwidth B and the quality factor Q is obtained by substituting Eq. (14.33) into Eq. (14.35) and utilizing Eq. (14.38).

$$B = \frac{R}{L} = \frac{\omega_0}{Q}$$

$$\omega_1 \approx \omega_0 - \frac{B}{2}, \quad \omega_2 \approx \omega_0 + \frac{B}{2}$$

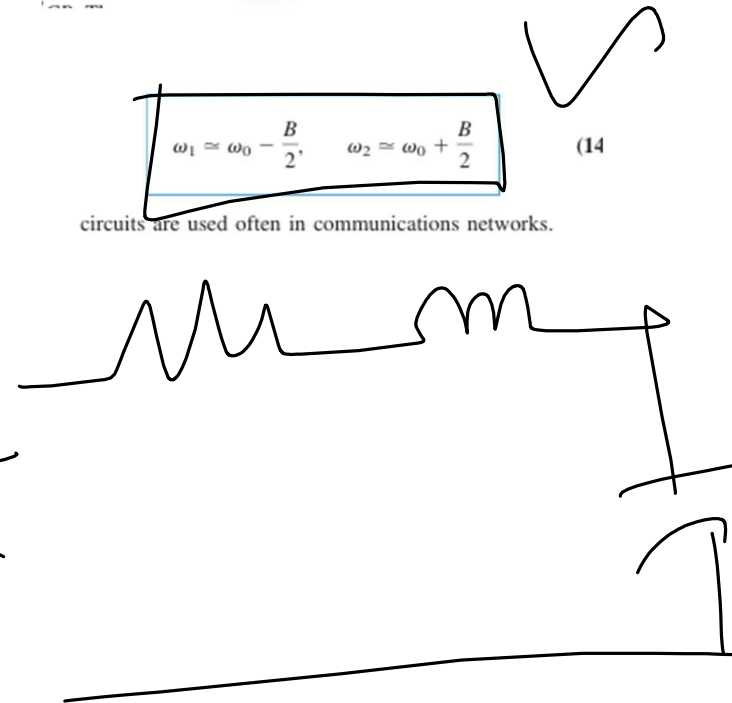Such circuits are used often in communications networks.



$$Q = \frac{W_0 L^2}{R}$$

$$W_0 = \frac{QR}{L}$$

$$= \frac{50 \times 4}{25 \times 10^{-3}}$$

$$= 8 \times 10^3 \text{ rad/s}$$

$$Q = \frac{1}{\omega CR}$$

$$C = \frac{1}{Q \omega R}$$

$$= 0.625 \mu F.$$

(ii)

$$B = \frac{R}{L}$$

$$= \frac{4}{25\text{m}}$$

$$= 160 \text{ rad/s}$$

$$w_1 = w_0 - \frac{B}{2 \times 10^3}$$

$$w_2 = w_0 + \frac{B}{2 \times 10^3}$$

$$(iii) \quad w = w_p = \frac{V^2}{2R}$$

$$= 1250 \text{ W.}$$

$w = w_1, w_2$ in half freq
at half freq. power is halved

$$\therefore p = \frac{1}{2} \times 1250 = 625 \text{ W.}$$

$$\frac{V^2}{R}$$

Parallel Resonance

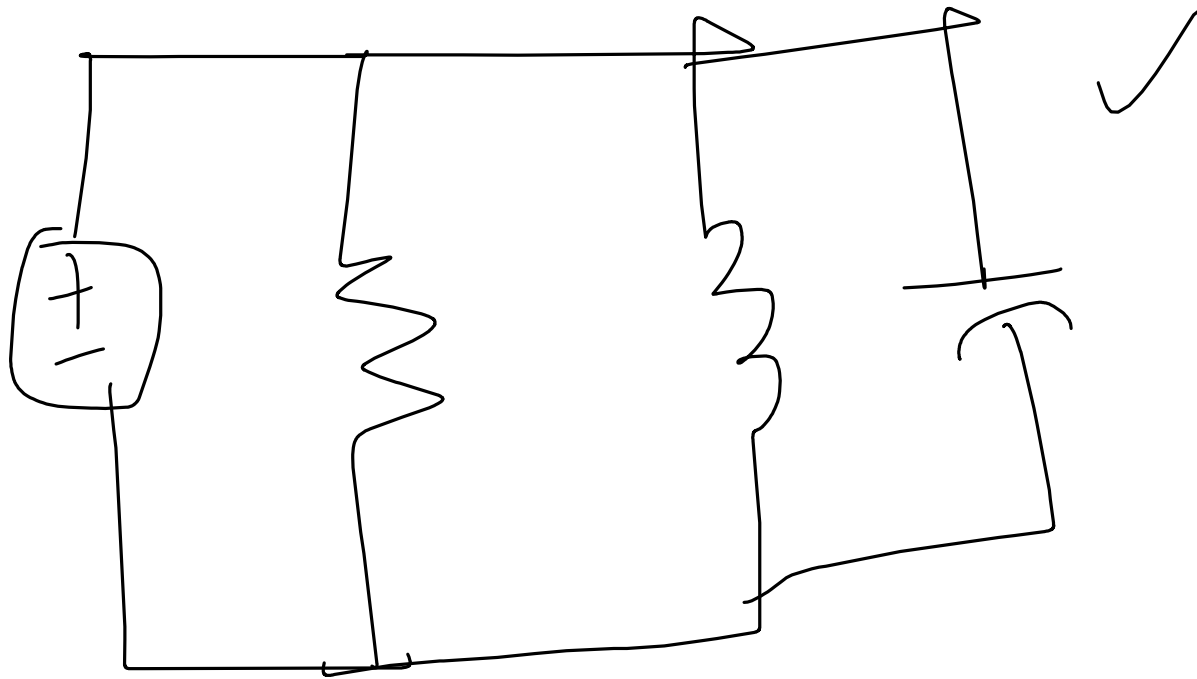


TABLE 14.4

Summary of the characteristics of resonant RLC circuits.

Characteristic	Series circuit	Parallel circuit
✓ Resonant frequency, ω_0	$\frac{1}{\sqrt{LC}}$	$\frac{1}{\sqrt{LC}}$
Quality factor, Q	$\frac{\omega_0 L}{R}$ or $\frac{1}{\omega_0 RC}$	$\frac{R}{\omega_0 L}$ or $\omega_0 RC$
Bandwidth, B	$\frac{\omega_0}{Q}$	$\frac{\omega_0}{Q}$
Half-power frequencies, ω_1, ω_2	$\omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{\omega_0}{2Q}$	$\omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{\omega_0}{2Q}$
For $Q \geq 10$, ω_1, ω_2	$\omega_0 \pm \frac{B}{2}$	$\omega_0 \pm \frac{B}{2}$

Practice Problem 14.8

A parallel resonant circuit has $R = 100 \text{ k}\Omega$, $L = 20 \text{ mH}$, and $C = 5 \text{ nF}$. Calculate ω_0 , ω_1 , ω_2 , Q , and B .

$$\omega_0 =$$

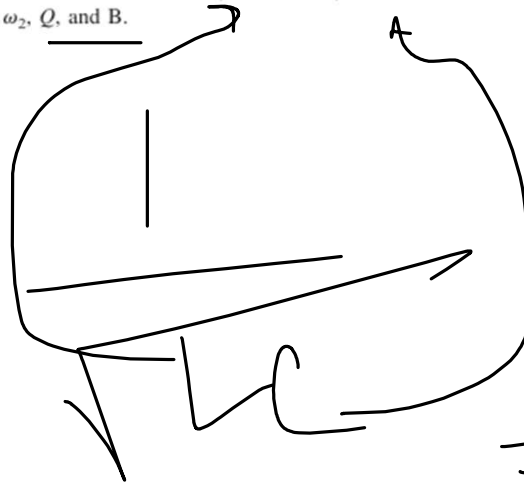


TABLE 14.4

Summary of the characteristics of resonant RLC circuits.

Characteristic	Series circuit	Parallel circuit
Resonant frequency, ω_0	$\frac{1}{\sqrt{LC}}$	$\frac{1}{\sqrt{LC}}$
Quality factor, Q	$\frac{\omega_0 L}{R}$ or $\frac{1}{\omega_0 RC}$	$\frac{R}{\omega_0 L}$ or $\omega_0 RC$
Bandwidth, B	$\frac{\omega_0}{Q}$	$\frac{\omega_0}{Q}$
Half-power frequencies, ω_1, ω_2	$\omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{\omega_0}{2Q}$	$\omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{\omega_0}{2Q}$
For $Q \geq 10$, ω_1, ω_2	$\omega_0 \pm \frac{B}{2}$	$\omega_0 \pm \frac{B}{2}$

$$= 1 \times 10^5 \text{ rad/s}$$

$$Q = \omega_0 RC$$

$$= 50$$

$$> 10$$

$$B = \frac{\omega_0}{Q} = 2000 \text{ rad/s}$$

$$\omega_1 = \omega_0 - \frac{\beta}{2}$$

$$= 1 \times 10^5 - 1000$$

$$\omega_2 = \omega_0 + \frac{\beta}{2}$$

$$= 1 \times 10^5 + 1000$$

Example 14.9

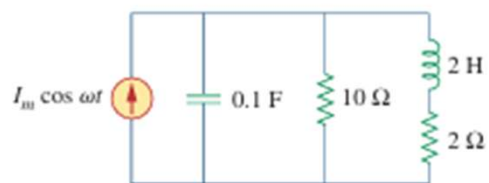


Figure 14.28
For Example 14.9.

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Find $Z = \text{Real} + j \text{Im}$.

$$\text{a) } \text{Im}(Z) = 0$$

$\omega_0 =$