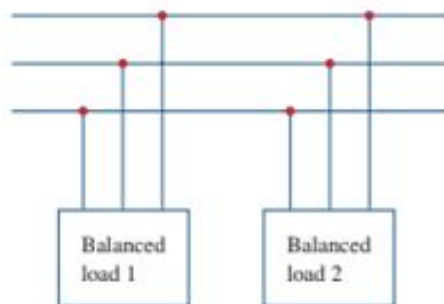


Practice Problem 12.8

Assume that the two balanced loads in Fig. 12.22(a) are supplied by an 840-V rms 60-Hz line. Load 1 is Y-connected with $30 + j40 \, \Omega$ per phase, while load 2 is a balanced three-phase motor drawing 48 kW at a power factor of 0.8 lagging. Assuming the *abc* sequence, calculate: (a) the complex power absorbed by the combined load, (b) the kVAR rating of each of the three capacitors Δ -connected in parallel with the load to raise the power factor to unity, and (c) the current drawn from the supply at unity power factor condition.



(a) given for load-1

$$V_1 = 840 \text{ V}$$

$$Z_L = 30 + j40$$

$$\begin{aligned} \bar{S}_{T_1} &= \frac{3V_p^2}{(30 - j40)} \quad \left| V_p = \frac{840}{\sqrt{3}} \right. \\ &= 8.5 \text{ k} + j11.3 \text{ k} \end{aligned}$$

for load-2

$$P_{T2} = 48 \text{ kW}$$

$$PF_2 = 0.8$$

$$P_{T2} = 3 V_p I_p \cos \theta$$

$$I_{T2} = \frac{3 V_p I_p}{PF_2} = \frac{P_{T2}}{0.8}$$

$$= 60 \text{ KVA}$$

$$\begin{aligned}
 Q_{T_2} &= S_{T_2} \sin \theta \\
 &= 60\text{K} \times \sin(37^\circ) \\
 &= 36.12\text{K}
 \end{aligned}$$

$$\begin{aligned}
 \theta &= \cos^{-1}(0.8) \\
 &= 37^\circ \checkmark
 \end{aligned}$$

$$\begin{aligned}
 S_{T_2} &= P_{T_2} + j Q_{T_2} \\
 &= 48\text{K} + j 36.12\text{K}
 \end{aligned}$$

$$\begin{aligned}
 \bar{S} &= \bar{S}_{T1} + \bar{S}_{T2} \\
 &= (16.5 \text{ k} + j 47.42 \text{ k}) \text{ VA}
 \end{aligned}$$

(b) From (a) we get,
 $Q = 47.42 \text{ kVAR}$

Change in
 Q ,

$$Q_c = Q - Q_L - 0 \quad \left[\text{To make pf} = 1, Q_L = 0 \right]$$
$$= Q \quad \therefore Q_c = Q$$

So the KVAR rating of the cap.

$$Q_{cap} = \frac{Q_C}{3}$$
$$= 15.8 \text{ KVAR}$$

(C)

$$\begin{aligned}\therefore S_T &= P_T + jQ_T \\ &= P_T + j0 \\ &= 56.5 \text{ kW} + j0 \\ &= \end{aligned}$$

$$\bar{S}_T = \sqrt{3} V_L I_L \cos \theta$$

$$= \sqrt{3} V_L I_L \cos 0^\circ$$

$$\therefore I_L = \frac{\bar{S}_T}{\sqrt{3} V_L}$$


$$= \frac{56.5 \text{ k}}{\sqrt{3} \times 840}$$

$$\theta = \cos^{-1}(1)$$

$$= 0^\circ$$


$$= 38.834 \text{ A}$$

Practice Problem 12.9

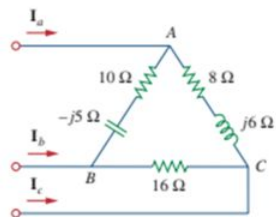

The unbalanced Δ -load of Fig. 12.24 is supplied by balanced line-to-line voltages of 440 V in the positive sequence. Find the line currents. Take V_{ab} as reference.
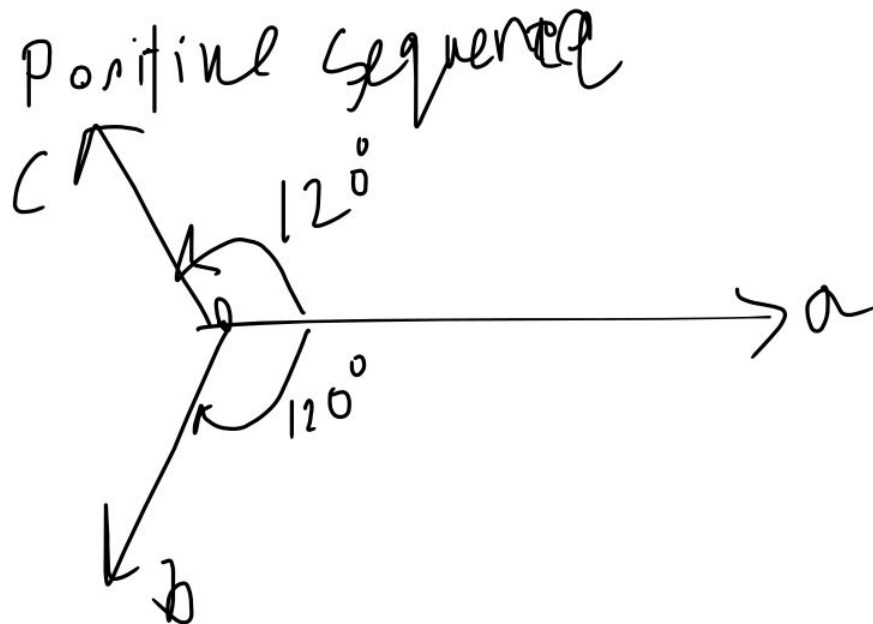
$$\left. \begin{aligned} V_{ab} &= 440 \angle 0^\circ \\ V_{bc} &= 440 \angle -120^\circ \\ V_{ca} &= 440 \angle 120^\circ \end{aligned} \right\}$$



here, $V_{\phi_{ind}} = V_{ab}$ $V_{ca} = 440 \angle 180^\circ + 120^\circ$

$$\therefore I_a = \frac{V_{ab}}{10 - j5} + \frac{V_{ac}}{8 + j6}$$

$$= \frac{440 \angle 0^\circ}{10 - j5} + \frac{440 \angle 308^\circ}{8 + j6}$$

$$= 39.71 \angle -41.06^\circ$$

$$\begin{aligned}
 I_b &= \frac{V_{bc}}{16} + \frac{V_{ba}}{10 - 5j} \quad | \quad V_{ba} = 440 \angle 180^\circ \\
 &= \frac{440 \angle -120^\circ}{16} + \frac{440 \angle 180^\circ}{10 - 5j} \\
 &= -46.95 - j41.42 = 61.12 \angle -140^\circ
 \end{aligned}$$

$$\begin{aligned}
 I_L &= \frac{V_{cb}}{16} + \frac{V_{ca}}{8 + 6j} \\
 &= \frac{440 \angle 60^\circ}{16} + \frac{440 \angle 120^\circ}{8 + 6j} \\
 &= 70.13 \angle 79.27^\circ
 \end{aligned}$$

$$\begin{aligned}
 V_{cb} &= -V_{bc} \\
 &= 440 \angle (190^\circ - 120^\circ) \\
 &= 440 \angle 60^\circ
 \end{aligned}$$

Calculate the line current required for a 30-kW three-phase motor having a power factor of 0.85 lagging if it is connected to a balanced source with a line voltage of 440 V.

Practice Problem 12.7

here.

$$P = \sqrt{3} V_L I_L \cos \theta$$

$$\therefore I_L = \frac{P}{\sqrt{3} \times V_L \times \cos \theta} = 46.31 \text{ A}$$

$$P = 30 \text{ kW}$$

$$V_L = 440$$

$$\text{Pf} = \cos \theta = 0.85$$

For the Y-Y circuit in Practice Prob. 12.2, calculate the complex power at the source and at the load.

Practice Problem 12.6

Practice Problem 12.2

A Y-connected balanced three-phase generator with an impedance of $0.4 + j0.3 \Omega$ per phase is connected to a Y-connected balanced load with an impedance of $24 + j19 \Omega$ per phase. The line joining the generator and the load has an impedance of $0.6 + j0.7 \Omega$ per phase. Assuming a positive sequence for the source voltages and that $V_{an} = 120 \angle 30^\circ \text{ V}$, find: (a) the line voltages, (b) the line currents.

Solⁿ

$$I_p = \frac{120 \angle 30^\circ}{(0.4 + j0.3) + (0.6 + j0.7) + (24 + j19)}$$

$$= 3.71 - j0.56$$

$$|I_p| = 3.74$$

As the connection is $y-y$ no the same
current I_p will flow through the source
phase & load phase.

Complex power at source

$$= -3 \times \bar{V}_p \times \bar{I}_p$$

$$= -3 \times (120 \angle 30^\circ) \times (3.71 + 0.56j)$$

$$= -[1055.87 + 842.4j] \text{ VA}$$

power at the load.

$$\begin{aligned} S_L &= 3 \times |I_p|^2 \times Z_L \\ &= 3 \times (3.75)^2 \times (24 + j19) \\ &= (1013.52 + j802.37) \text{ VA} \end{aligned}$$