

*9.55 Find Z in the network of Fig. 9.62, given that $V_o = 4 \angle 0^\circ \text{ V}$.

ML

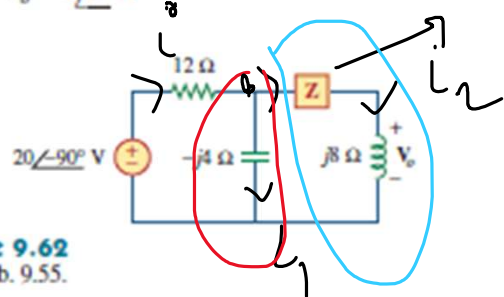


Figure 9.62
For Prob. 9.55.

$$i_2 = \frac{V_o}{j8} = \frac{4 \angle 0^\circ}{j8} = 0.5 \angle -90^\circ$$

$$V_{-j4} = i_2 (Z + j8)$$

$$\therefore i_1 = \frac{V_{-j4}}{-j4} = \frac{i_2 (Z + j8)}{-j4}$$

$$i = i_1 + i_2$$

$$= 0.5 \angle -90^\circ +$$

$$\frac{0.5 \angle -90^\circ (Z + j8)}{-j4}$$

*9.55 Find Z in the network of Fig. 9.62, given that $V_o = 4 \angle 0^\circ$ V.

ML

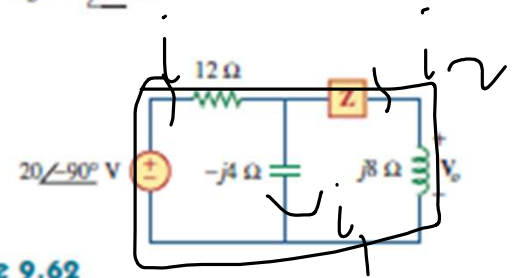


Figure 9.62
For Prob. 9.55.

KVL at outer loop,

*9.55 Find Z in the network of Fig. 9.62, given that $V_o = 4\angle 0^\circ$ V.

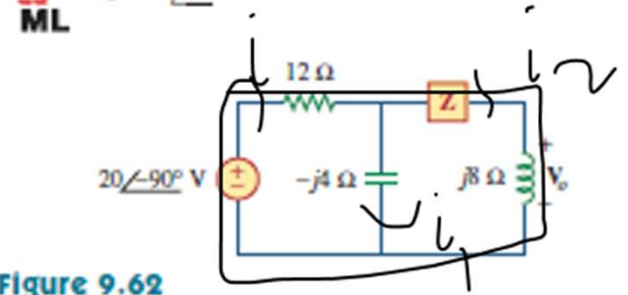


Figure 9.62
For Prob. 9.55.

$$-20\angle -90^\circ + i \times 12 + i_2(z + j8) = 0$$

$$\Rightarrow \frac{(0.5\angle -90^\circ)(z + j8)}{-j4} = \frac{12 + 0.5\angle -90^\circ(z + j8)}{20\angle -90^\circ}$$

$$\Rightarrow \frac{1}{8} \times (z + j12) \times 12 + 0.5 \angle -90^\circ z + 4$$

$$= 2 \angle 90^\circ$$

$$\Rightarrow 1.5z + j12 + 0.5 \angle -90^\circ z + 4$$

$$= 2 \angle -90^\circ$$

$$\Rightarrow Z(1.5 + 0.5 \angle -90^\circ) = 20 \angle -90^\circ - 4 - j12$$

$$Z = 20.37 \angle -78.7^\circ \checkmark$$

9.66 For the circuit in Fig. 9.73, calculate Z_T and V_{ab} .

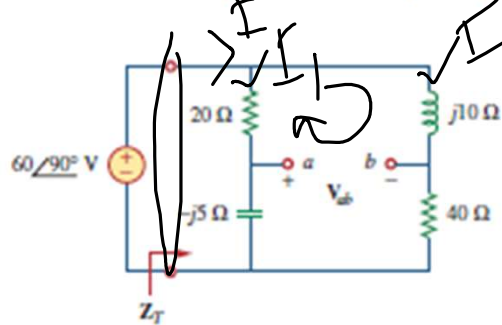


Figure 9.73
For Prob. 9.66.

$$Z_T = (20 - j5) \parallel (40 + j10)$$

$$I = \frac{60 \angle 90^\circ}{Z_T} = 14.12 \angle -4.8^\circ$$

$$= 4.25 \angle 94.8^\circ$$

$$I_1 = I \times \frac{40 + j10}{60 + 5j}$$

$$= 2.91 \angle 104.07^\circ$$

$$I_2 = \frac{20 \angle -90^\circ - j5}{60 + 5j} \times I$$

$$= 1.45 \angle 76^\circ$$

9.66 For the circuit in Fig. 9.73, calculate Z_T and V_{ab} .

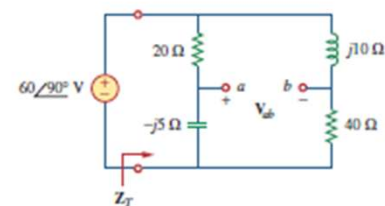


Figure 9.73
For Prob. 9.66.

$$\frac{KVL}{-V_{ab} - 20 \times I_1 + j10 I_2}$$

$$= 0$$

$$\Rightarrow V_{ab} = -20 I_1 - j10 \times I_2$$

$$=$$

9.66 For the circuit in Fig. 9.73, calculate Z_T and V_{ab} .

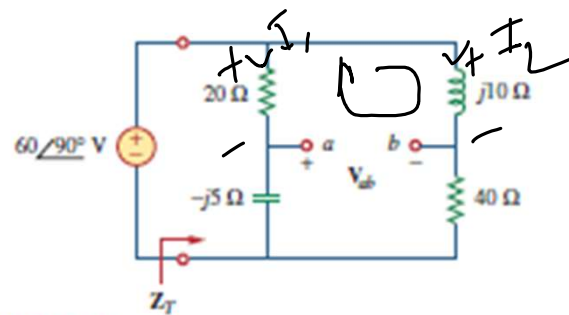


Figure 9.73
For Prob. 9.66.

9.63 For the circuit in Fig. 9.70, find the value of Z_T .

ML

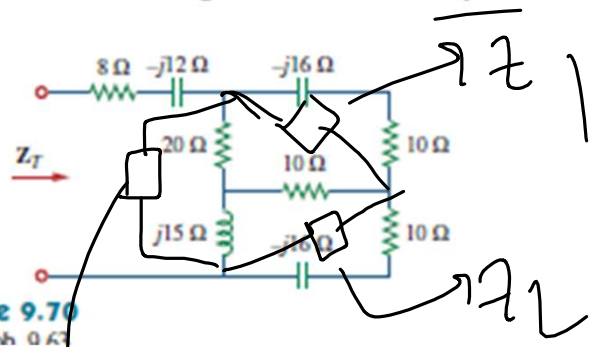


Figure 9.70
File Dsch 0.63

9.63 For the circuit in Fig. 9.70, find the value of Z_T .

ML

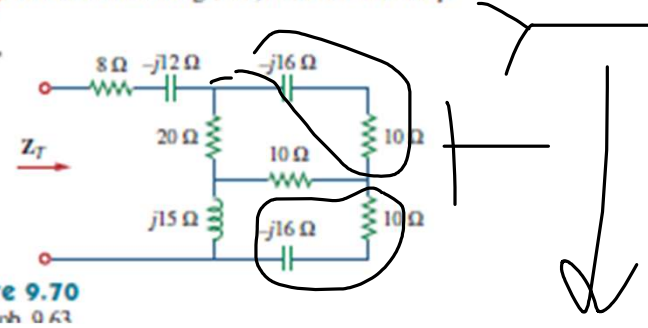


Figure 9.70
File Dsch 0.63

$$Z_1 = \frac{20 \times 10 + 10 \times j15 + j15 \times 20}{j15}$$



$$= 32.83 \angle -23.96^\circ$$

$$20 + 450j$$

$$z_2 = \frac{200 + 450j}{10}$$

$$= 20 \angle 66^\circ$$
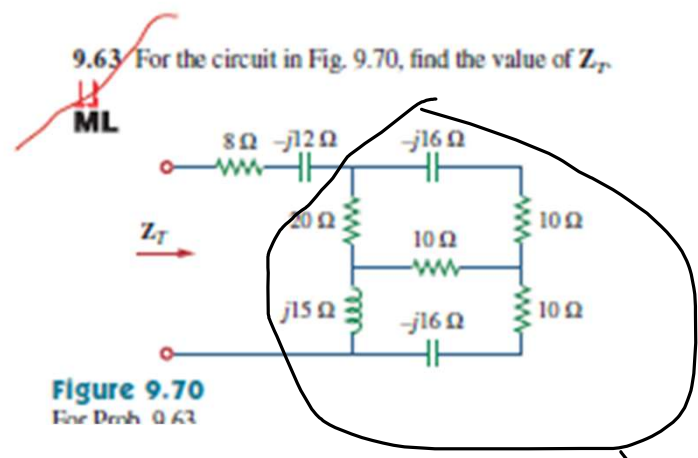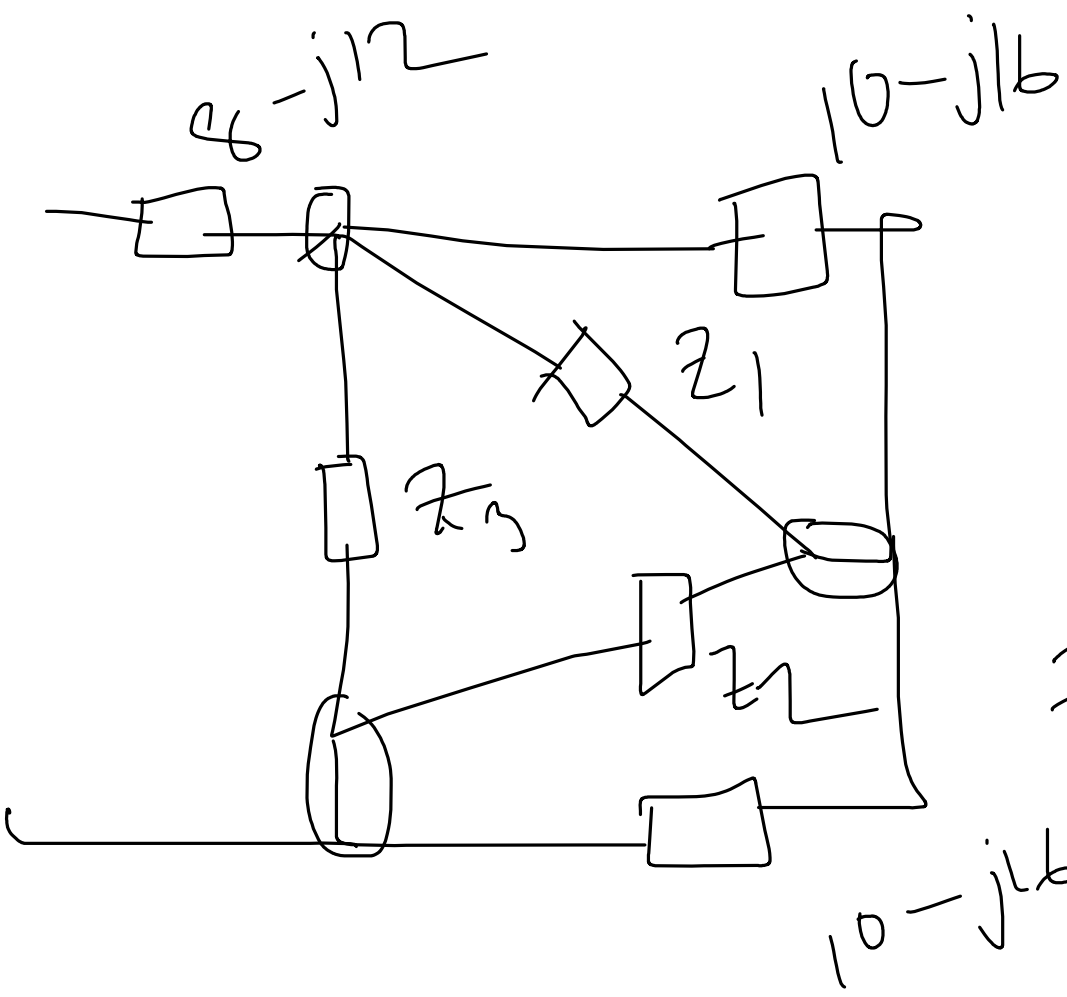
$$z_3 = \frac{200 + 450j}{10} = 49.24 \angle 66^\circ$$




$$Z_{S1} = Z_1 \parallel (10 - j16)$$

$$= 12.48 \angle -45^\circ$$

$$Z_{S2} = Z_2 \parallel (10 - j16)$$

$$= 23.5 \angle -56.4^\circ$$

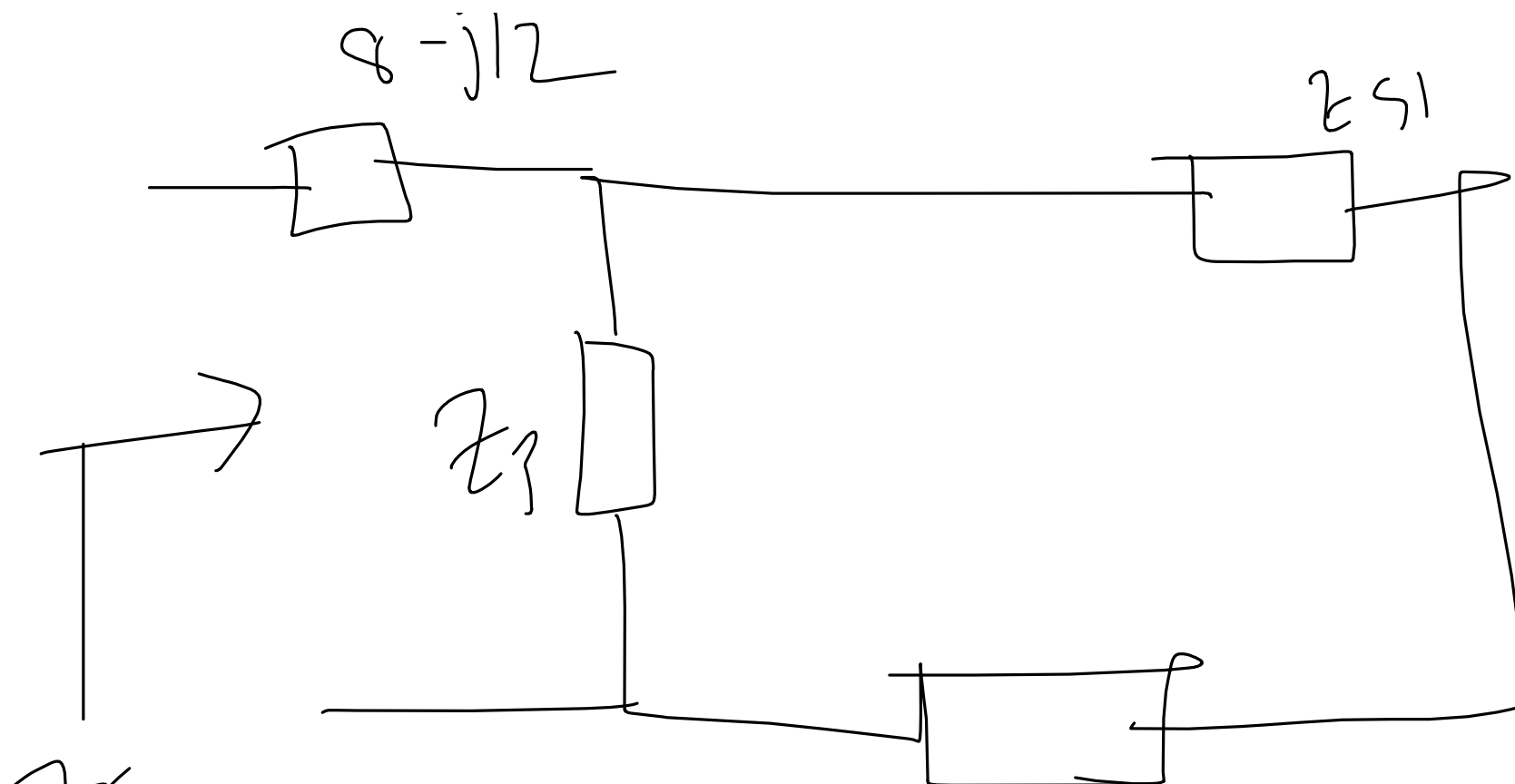


$$Z_T = (8-j12) + Z_3 \parallel (Z_{S1} + Z_{S2})$$

Nodal Analysis

5 steps

- (1) find nodes
 + node $\rightarrow$ ref node
 rest are non-ref nodes
- (2) Apply KCL to the non-ref nodes

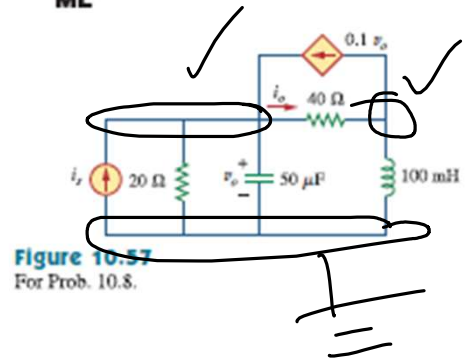10.8 Use nodal analysis to find current i_o in the circuit of Fig. 10.57. Let $i_s = 6 \cos(200t + 15^\circ)$ A.



③ Solⁿ KCL eqⁿ

$$\frac{KCL-1}{50 \mu F \rightarrow \frac{1}{j \times 200 \times 50 \mu}} \quad \omega = 200$$

$$\dot{I}_s = 6 \angle 15^\circ$$

$$6 \angle 15^\circ + 0.1 V_o = \frac{V_1}{20} + \frac{V_1}{-j100} + \frac{V_1 - V_2}{40}$$

$$V_o = V_1$$

10.8 Use nodal analysis to find current i_o in the circuit of Fig. 10.57. Let $i_s = 6 \cos(200t + 15^\circ)$ A.

ML

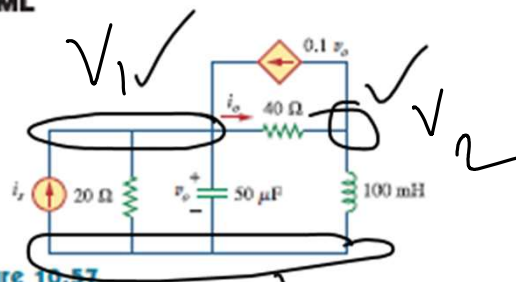


Figure 10.57
For Prob. 10.8.

$\omega = 200$

$$6/15^6 = \frac{1}{20} - \frac{1}{j100} + \frac{1}{40 - 0.1j}$$

$$= \frac{\sqrt{2}}{40}$$

①

KCL-2

$$v_o = V_1$$

$$100 \text{ mH} \rightarrow j\omega(100 \text{ m}) = -j20$$

$$0.1V_1 + \frac{V_2}{j20} = -\frac{V_1 - V_2}{40}$$

$$\Rightarrow V_1 \left(0.1 - \frac{1}{40} \right) + V_2 \left(\frac{1}{j20} + \frac{1}{40} \right) = 0 \quad \text{--- (2)}$$

10.8 Use nodal analysis to find current i_o in the circuit of Fig. 10.57. Let $i_s = 6 \cos(200t + 15^\circ)$ A.

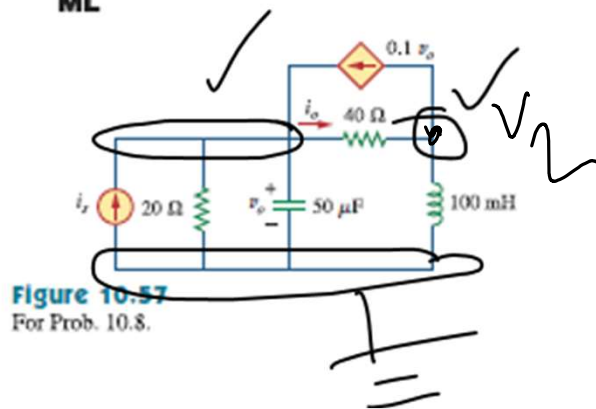


Figure 10.57
For Prob. 10.8.

$$i_0 = \frac{V_1 - V_2}{40}$$

Solving


eqⁿ (1) & (2),

$$V_1 = 143.52 \angle -120^\circ$$

$$V_2 = 195.2 \angle 25^\circ$$

$$i_o = \frac{V_1 - V_L}{410}$$

$$= 1.302 \angle -41^\circ$$

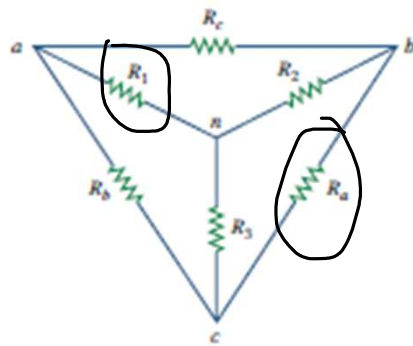

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$