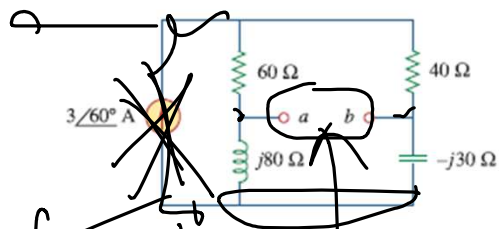


10.64 For the circuit shown in Fig. 10.107, find the Norton equivalent circuit at terminals $a-b$.



$3 \angle 60^\circ$

$$Z_{eq} = Z_N$$


$$Z_N = (60 + 40) \parallel (j80 - j30)$$

||

I_N

By applying mesh analysis.

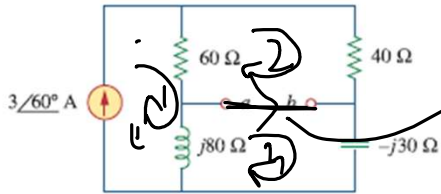10.64 For the circuit shown in Fig. 10.107, find the Norton equivalent circuit at terminals $a-b$.



$I_{sc} = I_N$


$I_1 = 3 \angle 60^\circ$

$I_2 = \dots$

$I_3 = \dots$

$I_N = I_3 - I_2$

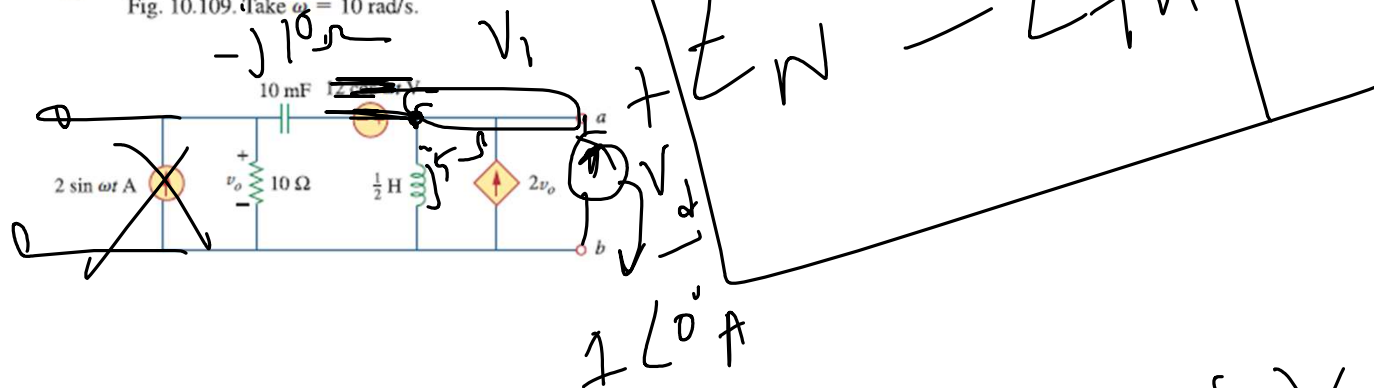10.66 At terminals $a-b$, obtain Thevenin and Norton equivalent circuits for the network depicted in Fig. 10.109. Take $\omega = 10$ rad/s.



applying KCL at node of V_1

$$\frac{V_1}{10 - j10} + \frac{V_1}{5j} - 2 \times (\sqrt{2} \angle 45^\circ) V_1 - 1 \angle 0^\circ = 0$$

$$V_0 = V_{10\Omega} = \frac{10}{10 - j10} \times V_1$$

$$= (\sqrt{2} \angle 45^\circ) V_1$$


$$V_1 = \frac{1 \angle 0^\circ}{\left(\frac{1}{10 - j10} + \frac{1}{5j} - 2\sqrt{2} \angle 45^\circ \right)}$$

$$V_1 = V_d$$

$$Z_N = \frac{V_d}{1 \angle 0^\circ}$$

$$I_N = \frac{V_{th}}{Z_N}$$

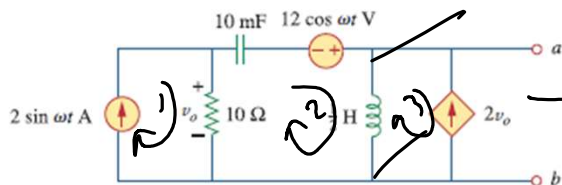10.66 At terminals $a-b$, obtain Thevenin and Norton equivalent circuits for the network depicted in Fig. 10.109. Take $\omega = 10$ rad/s.




$$I_1 = \frac{2 \angle 0^\circ}{2 \angle 6} = -20(I_1 - I_2)$$

$$I_3 = -2 \angle 6 = -20(2 \angle 0 - I_1)$$

$$V_o = (I_1 - I_2) \times 10$$

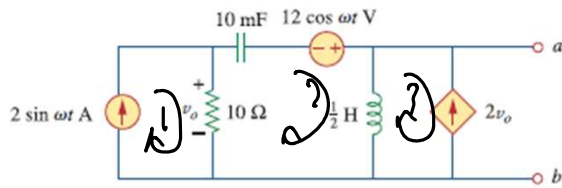10.66 At terminals $a-b$, obtain Thevenin and Norton equivalent circuits for the network depicted in Fig. 10.109. Take $\omega = 10 \text{ rad/s}$.



KVL at mesh-2


$$\begin{aligned}
 (10 - j10) \times (I_2 - I_1) - 12 \angle 0^\circ + j5 \times (I_2 - I_3) \\
 \Rightarrow (10 - j10) \times (I_2 - 2 \angle 0^\circ) - 12 \angle 0^\circ + j5 \times \\
 (I_2 + 2 \angle 0^\circ - I_2) \\
 = 0
 \end{aligned}$$

$$I_2(10 - j10) - 2\angle 6^\circ(10 - j10) - 12\angle 0^\circ$$

$$+ j5 I_2 + 46\angle 0^\circ - 20I_2 = 0$$

$$\therefore I_2 = \frac{21\angle 68^\circ}{30\angle -9.46^\circ} = 0.7\angle 80^\circ$$

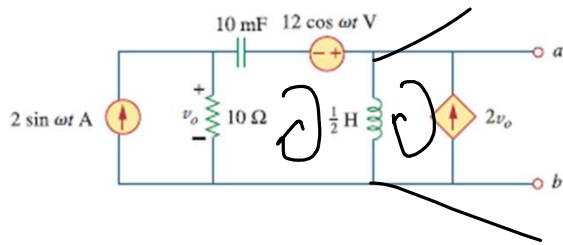10.66 At terminals $a-b$, obtain Thevenin and Norton equivalent circuits for the network depicted in Fig. 10.109. Take $\omega = 10$ rad/s.



$$I_3 = -20(2\angle 0^\circ - I_2)$$




$$= 40\angle 16^\circ$$

$$V_{th} = (I_2 - I_3) \times j5 = 200\angle 71^\circ \text{ V}$$

$$I_N = \frac{V_{th}}{Z_N}$$

Superposition theorem


We turn off only the independent source.

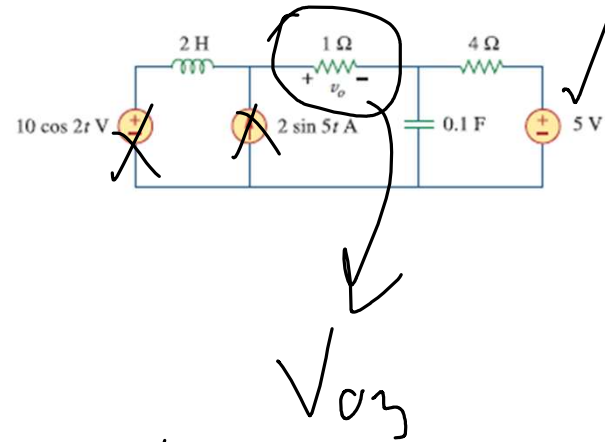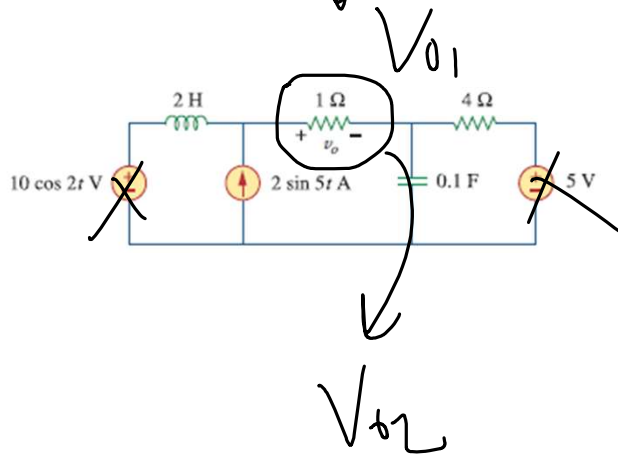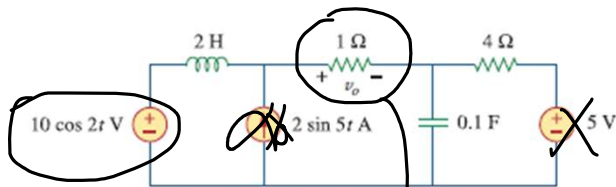

$$V_o = V_{01} + V_{02} + V_{03}$$

i_{o1}

i_{o2}



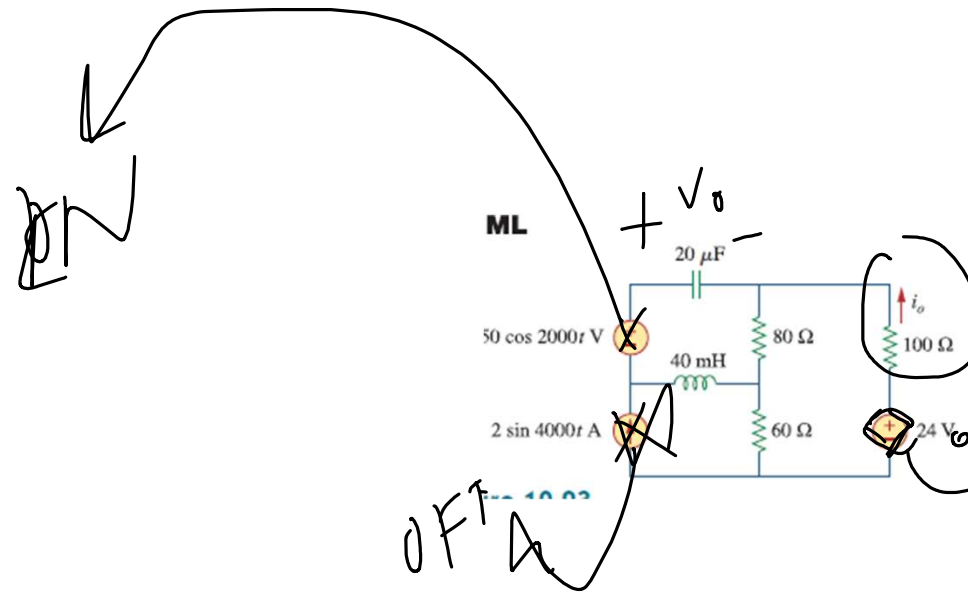




suppne it in
a dependent
voltage
source

In superposition
you cannot turn off the


dependent
source

Source Transformation

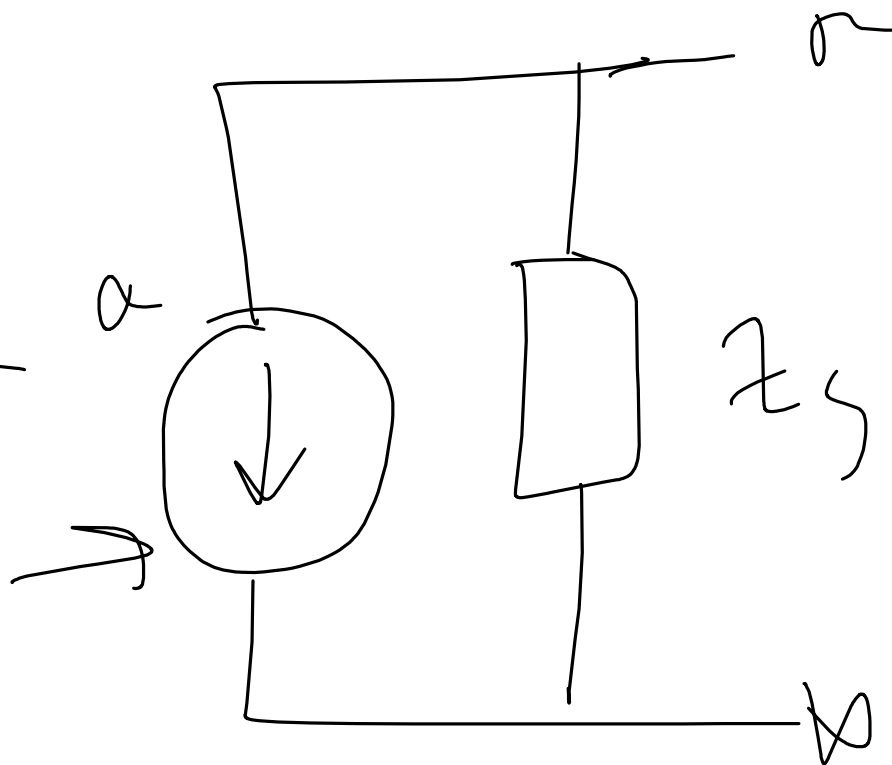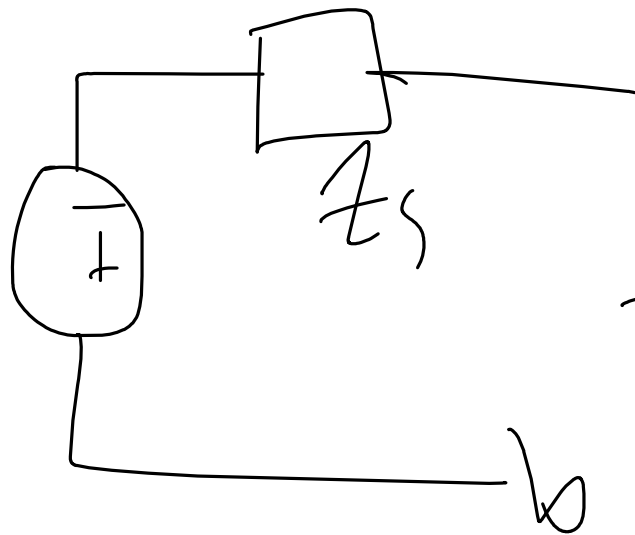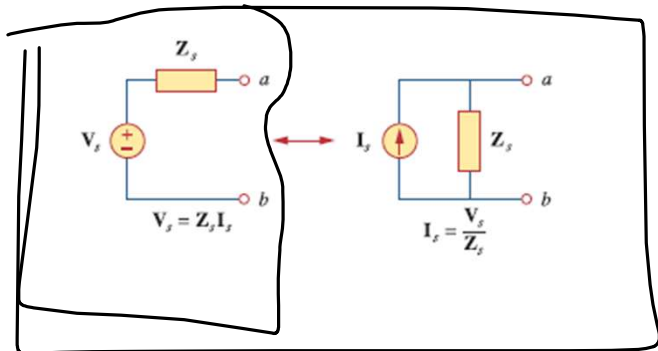


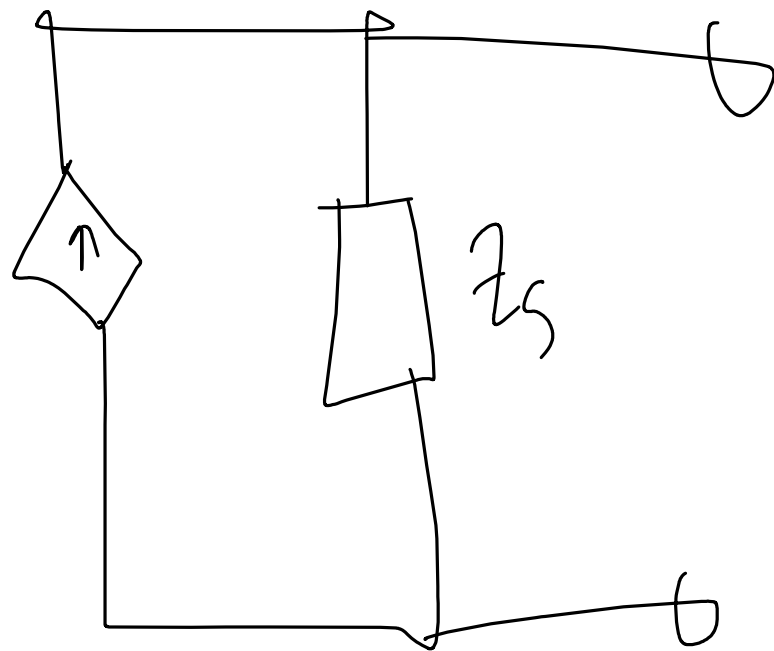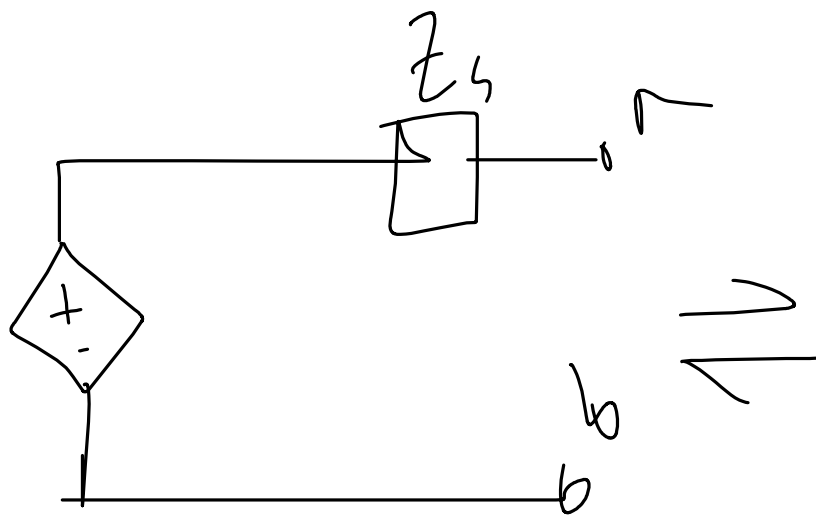

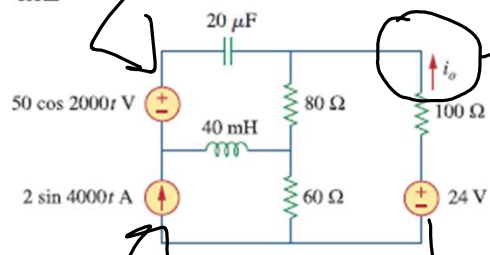10.48 Find i_o in the circuit of Fig. 10.93 using superposition.



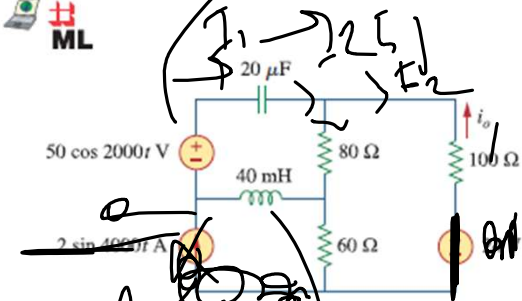10.48 Find i_o in the circuit of Fig. 10.93 using superposition.



$$Z_T = (100 + 60) \parallel 80 + (j80 - j25)$$

$$20 \mu F \rightarrow$$

$$= \frac{1}{\frac{1}{2000 \times 20 \mu F}} = 25 \Omega$$


$$I_1 = \frac{50 \angle 0^\circ}{Z_T}$$

$$I_2 = I_1 \times \frac{80}{160 + 80}$$

$$I_{op} = -I_2$$

$$\boxed{I_{op}}$$

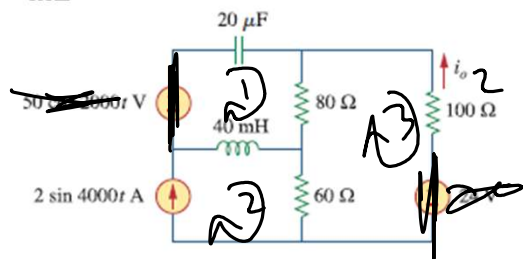10.48 Find i_o in the circuit of Fig. 10.93 using superposition.



i_o



Applying mesh

I_1
 I_2
 I_3

$$I_o = -I_3$$

i_o

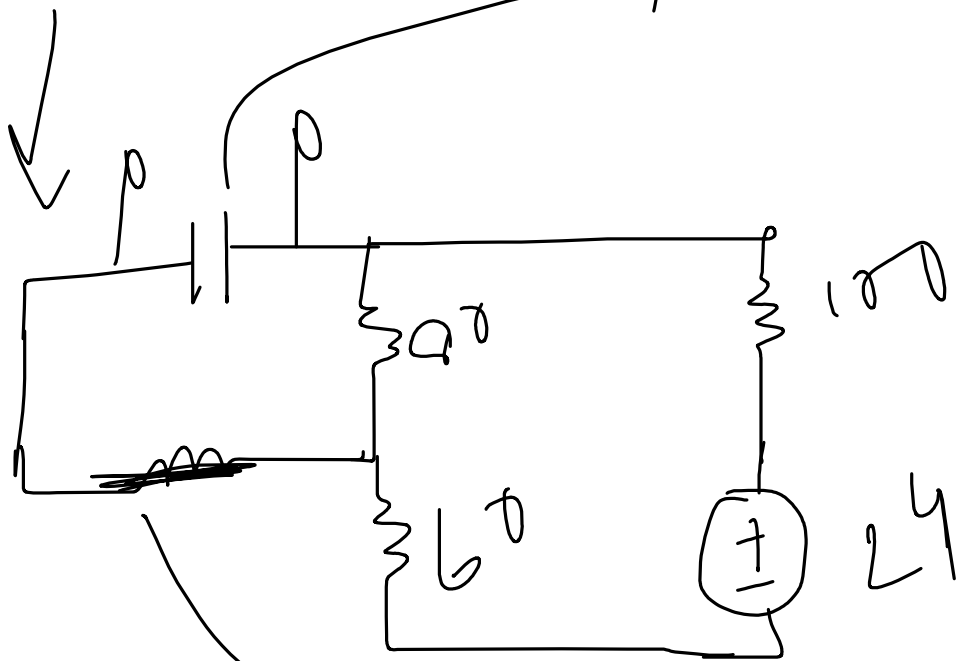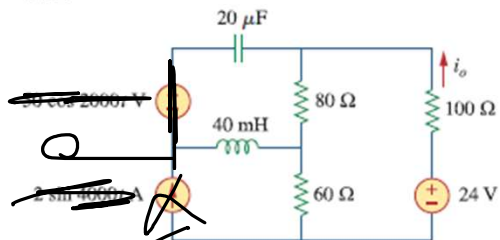10.48 Find i_o in the circuit of Fig. 10.93 using superposition.



$$20 \mu F \rightarrow \frac{1}{2\pi f \times 20 \mu F} = \infty$$

$$40 \text{ mH} \rightarrow \frac{1}{2\pi f \times 40 \text{ mH}} = 0$$

$$i_{o3} = \frac{24}{240} \text{ A}$$

$$= 0.1 \text{ A}$$

$$i_o = i_{o1} + i_{o2} + i_{o3}$$